

# PROJECT REPORT


Parsa KafshduziBukani

CA6


# Data Paths

Persa Kafshlouei Bukhari 810102501 CA 6

Data Path:

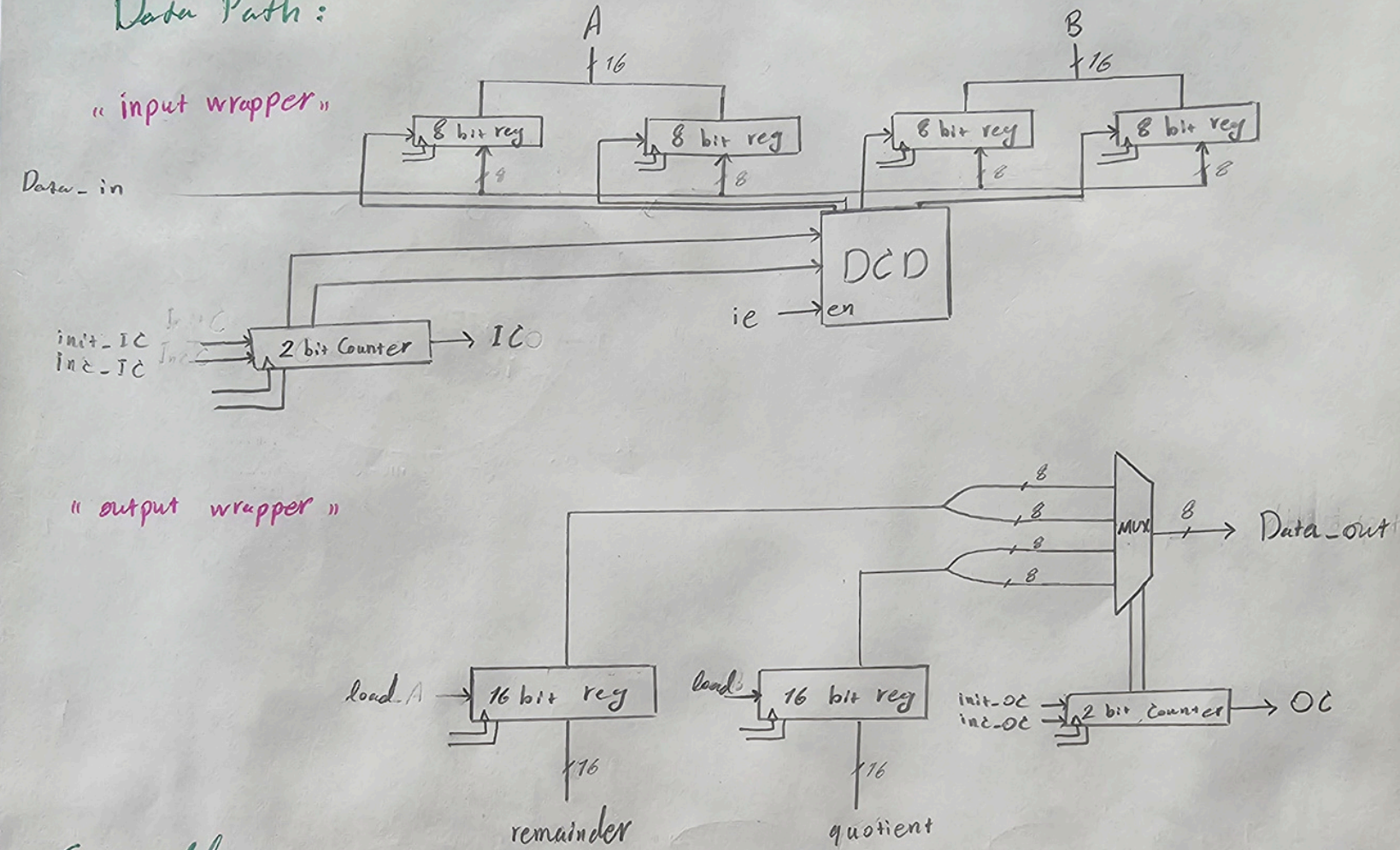


Controller:

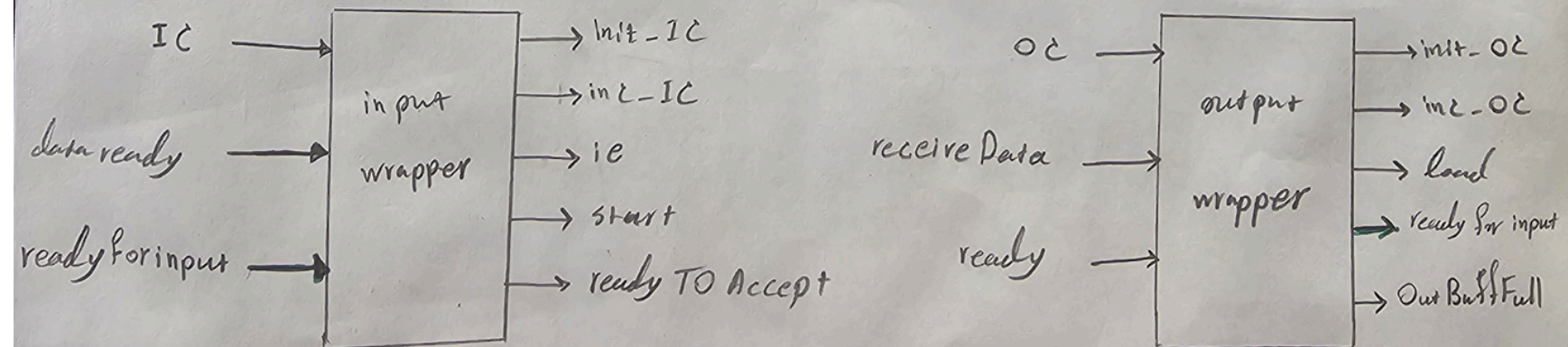




# Controllers


## Input Wrapper:

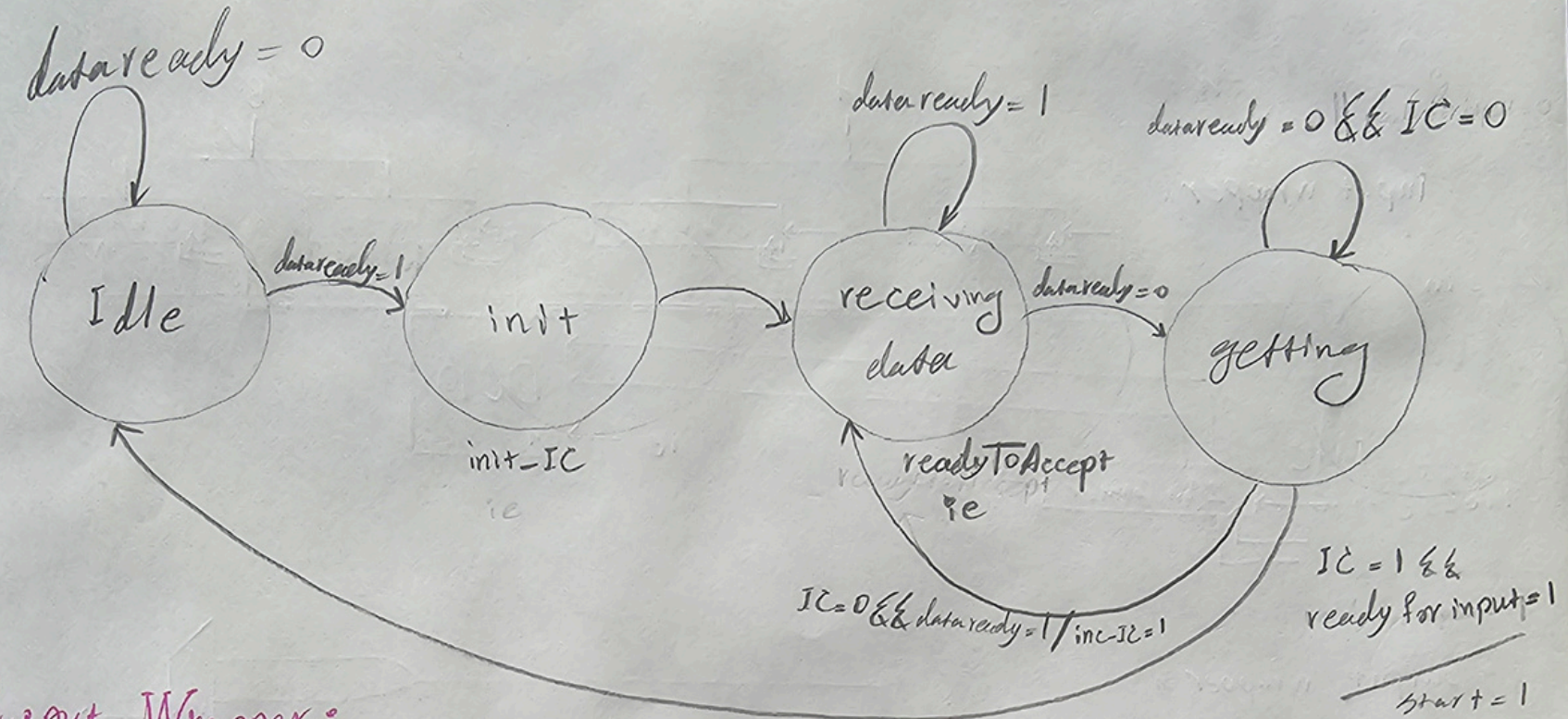

## Output Wrapper:

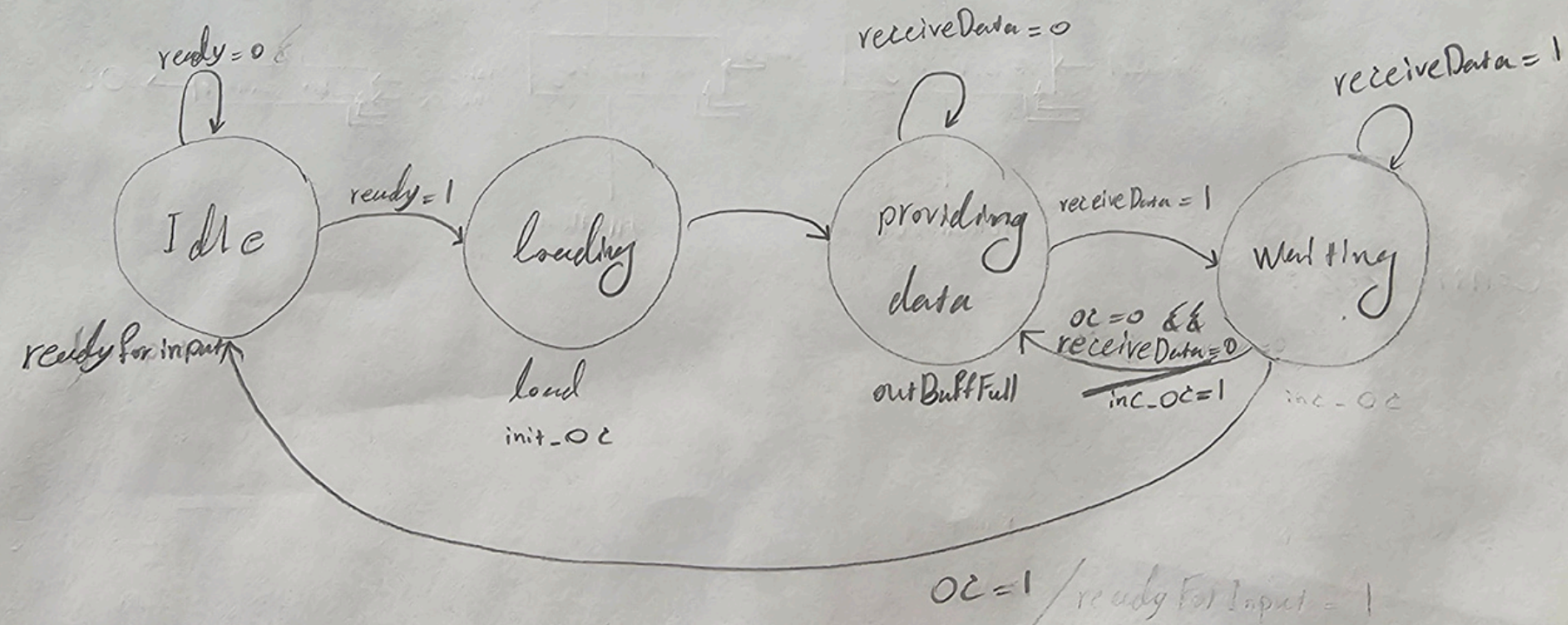

# Signals

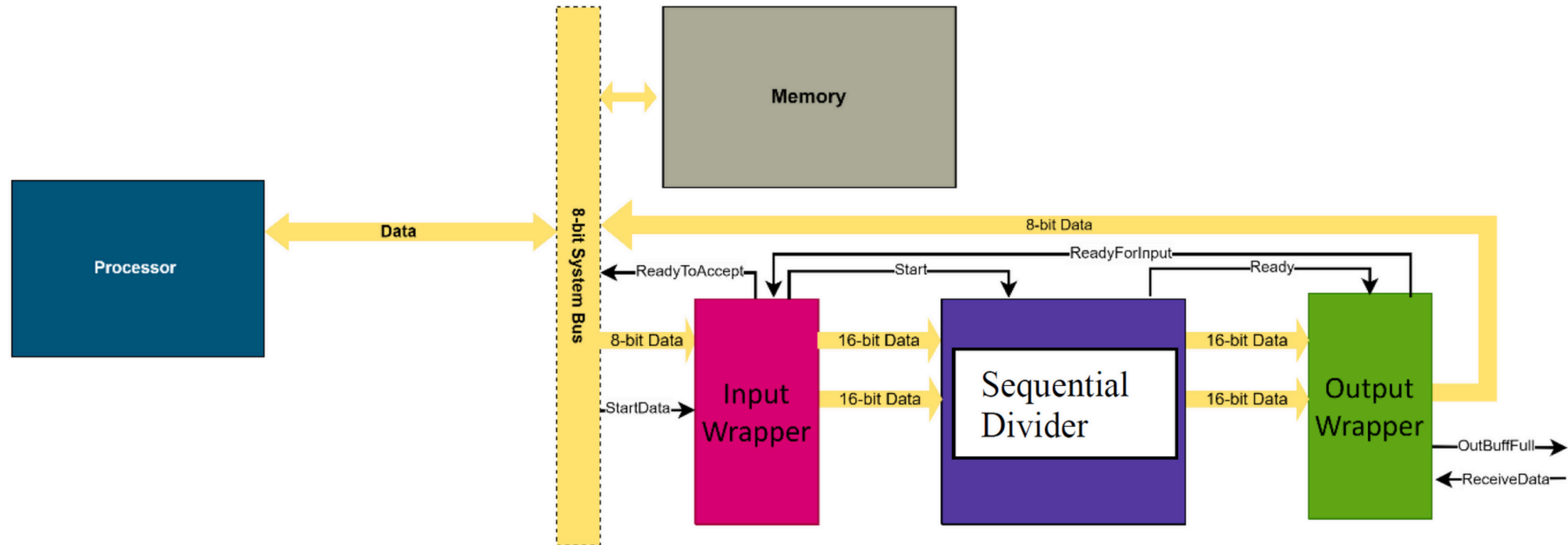



# Sequential Divider

The controller and data path of the sequential divider were provided in CA5

```
module sequentialDivider (  
    input clk,  
    input rst,  
    input start,  
    input [15:0] A,  
    input [15:0] B,  
    output [15:0] Quotient,  
    output [15:0] Remainder,  
    output ready,  
    output error  
);  
  
wire load_A, load_B, sh1, sh2, inz_0, load_sub;  
wire cout;  
wire [15:0] Re;  
  
Controller_SequentialDivider controller (  
    .clk(clk),  
    .rst(rst),  
    .start(start),  
    .Re(Re),  
    .cout(cout),  
    .error(error),  
    .load_A(load_A),  
    .load_B(load_B),  
    .sh1(sh1),  
    .sh2(sh2),  
    .inz_0(inz_0),  
    .load_sub(load_sub),  
    .ready(ready)  
);  
  
SequentialDivider_Datapath sequential_divider (  
    .A(A),  
    .B(B),  
    .load_A(load_A),  
    .load_B(load_B),  
    .sh1(sh1),  
    .sh2(sh2),  
    .inz_0(inz_0),  
    .load_sub(load_sub),  
    .rst(rst),  
    .clk(clk),  
    .Quotient(Quotient),  
    .Remainder(Remainder),  
    .Re(Re),  
    .cout(cout),  
    .error(error)  
);  
  
endmodule
```

# Input Wrapper

```
module inputWrapper_Datapath (  
    input clk, rst,  
    input [7:0] Data_in,  
    input init_IC,  
    input inc_IC,  
    input ie,  
    output reg [15:0] A,  
    output reg [15:0] B,  
    output IC  
);  
  
reg [1:0] count;  
reg [7:0] A1, A2, B1, B2;  
  
always @(posedge clk or posedge rst) begin  
    if (rst) begin  
        A1 <= 0; A2 <= 0;  
        B1 <= 0; B2 <= 0;  
    end  
    else if (ie) begin  
        case (count)  
            2'b00: A1 <= Data_in;  
            2'b01: A2 <= Data_in;  
            2'b10: B1 <= Data_in;  
            2'b11: B2 <= Data_in;  
        endcase  
    end  
end  
  
always @(posedge clk or posedge rst) begin  
    if (rst)  
        count <= 2'b00;  
    else if (init_IC)  
        count <= 2'b00;  
    else if (inc_IC)  
        count <= count + 1;  
end  
  
assign IC = &count;  
assign A = {A2, A1};  
assign B = {B2, B1};  
  
endmodule
```

```
module Controller_inputWrapper (  
    input clk, rst,  
    input IC,  
    input dataready,  
    input readyforinput,  
    output reg init_IC,  
    output reg inc_IC,  
    output reg ie,  
    output reg start,  
    output reg readyToAccept  
);  
  
parameter [1:0] idle = 2'b00, init = 2'b01, receiving_data = 2'b11, getting = 2'b10;  
reg [1:0] pstate, nstate;  
  
always @(pstate, readyforinput, IC, dataready) begin  
    nstate = 2'b0;  
    {init_IC, inc_IC, ie, start, readyToAccept} = 5'b00000;  
  
    case(pstate)  
        idle: nstate = dataready ? init : idle;  
        init: begin  
            {init_IC, ie} = 2'b11;  
            nstate = receiving_data;  
        end  
        receiving_data: begin  
            {readyToAccept, ie} = 2'b11;  
            nstate = dataready ? receiving_data : getting;  
        end  
        getting: begin  
            start = (IC & readyforinput) ? 1 : 0;  
            inc_IC = (~IC & dataready) ? 1 : 0;  
            nstate = (~IC & dataready) ? receiving_data :  
                (~dataready & ~IC) ? getting :  
                idle;  
        end  
    endcase  
end  
  
always @(posedge clk or posedge rst) begin  
    if (rst)  
        pstate <= idle;  
    else  
        pstate <= nstate;  
    end  
end  
  
endmodule
```

```
module inputWrapper (  
    input clk, rst,  
    input [7:0] Data_in,  
    input dataready, readyforinput,  
    output [15:0] A, B,  
    output start, readyToAccept  
);  
  
wire init_IC, inc_IC, ie, IC;  
  
inputWrapper_Datapath datapath (  
    .clk(clk),  
    .rst(rst),  
    .Data_in(Data_in),  
    .init_IC(init_IC),  
    .inc_IC(inc_IC),  
    .ie(ie),  
    .A(A),  
    .B(B),  
    .IC(IC)  
);  
  
Controller_inputWrapper controller (  
    .clk(clk),  
    .rst(rst),  
    .IC(IC),  
    .dataready(dataready),  
    .readyforinput(readyforinput),  
    .init_IC(init_IC),  
    .inc_IC(inc_IC),  
    .ie(ie),  
    .start(start),  
    .readyToAccept(readyToAccept)  
);  
  
endmodule
```

# output Wrapper

```
module outputWrapper_Datapath (
    input clk, rst,
    input [15:0] remainder,
    input [15:0] quotient,
    input init_OC,
    input inc_OC,
    input load,
    output reg [7:0] Data_out,
    output OC
);

reg [1:0] count;
reg [15:0] Quotient_reg;
reg [15:0] Remainder_reg;

always @(posedge clk or posedge rst) begin
    if (rst) begin
        Quotient_reg = 0;
        Remainder_reg = 0;
    end
    else if (load) begin
        Quotient_reg = quotient;
        Remainder_reg = remainder;
    end
end

always @(posedge clk or posedge rst) begin
    if (rst)
        count <= 2'b00;
    else if (init_OC)
        count <= 2'b00;
    else if (inc_OC)
        count <= count + 1;
end

assign Data_out = (count == 2'b00) ? Quotient_reg[7:0] :
                  (count == 2'b01) ? Quotient_reg[15:8] :
                  (count == 2'b10) ? Remainder_reg[7:0] :
                  (count == 2'b11) ? Remainder_reg[15:8] : 8'bz;

assign OC = &count;

endmodule
```

```
module Controller_outputWrapper (
    input clk, rst,
    input OC,
    input receiveData,
    input ready,
    output reg init_OC,
    output reg inc_OC,
    output reg load,
    output reg readyforinput,
    output reg OutBuffFull
);

parameter [1:0] idle = 2'b00, loading = 2'b01, providing_data = 2'b11, waiting = 2'b10;
reg [1:0] pstate, nstate;

always @(pstate, ready, OC, receiveData) begin
    nstate = 2'b0;
    {init_OC, inc_OC, load, OutBuffFull, readyforinput} = 5'b00000;

    case(pstate)
        idle: begin
            readyforinput = 1;
            nstate = ready ? loading : idle;
        end
        loading: begin
            {init_OC, load} = 2'b11;
            nstate = providing_data;
        end
        providing_data: begin
            OutBuffFull = 1;
            nstate = receiveData ? waiting : providing_data;
        end
        waiting: begin
            inc_OC = (~OC & ~receiveData) ? 1 : 0;
            nstate = OC ? idle :
                    (~OC & ~receiveData) ? providing_data :
                    waiting;
        end
    endcase
end

always @(posedge clk or posedge rst) begin
    if (rst)
        pstate <= idle;
    else
        pstate <= nstate;
    end
end

endmodule
```

```
module outputWrapper (
    input clk, rst,
    input [15:0] remainder, quotient,
    input receiveData, ready,
    output [7:0] Data_out,
    output OutBuffFull, readyforinput
);

wire init_OC, inc_OC, load, OC;

outputWrapper_Datapath datapath (
    .clk(clk),
    .rst(rst),
    .remainder(remainder),
    .quotient(quotient),
    .init_OC(init_OC),
    .inc_OC(inc_OC),
    .load(load),
    .Data_out(Data_out),
    .OC(OC)
);

Controller_outputWrapper controller (
    .clk(clk),
    .rst(rst),
    .OC(OC),
    .receiveData(receiveData),
    .ready(ready),
    .init_OC(init_OC),
    .inc_OC(inc_OC),
    .load(load),
    .readyforinput(readyforinput),
    .OutBuffFull(OutBuffFull)
);

endmodule
```

# System

```
module System (  
    input clk, rst,  
    input dataready,  
    input [7:0] Data_in,  
    input receiveData,  
    output [7:0] Data_out,  
    output OutBuffFull,  
    output error,  
    output readyToAccept  
);  
  
wire [15:0] A, B;  
wire ready, start;  
wire [15:0] remainder, quotient;  
wire readyforinput;  
  
inputWrapper input_wrapper (  
    .clk(clk),  
    .rst(rst),  
    .Data_in(Data_in),  
    .dataready(dataready),  
    .readyforinput(readyforinput),  
    .A(A),  
    .B(B),  
    .start(start),  
    .readyToAccept(readyToAccept)  
);  
sequentialDivider seq_divider (  
    .clk(clk),  
    .rst(rst),  
    .start(start),  
    .A(A),  
    .B(B),  
    .Quotient(quotient),  
    .Remainder(remainder),  
    .ready(ready),  
    .error(error)  
);  
outputWrapper output_wrapper (  
    .clk(clk),  
    .rst(rst),  
    .remainder(remainder),  
    .quotient(quotient),  
    .receiveData(receiveData),  
    .ready(ready),  
    .Data_out(Data_out),  
    .OutBuffFull(OutBuffFull),  
    .readyforinput(readyforinput)  
);  
endmodule
```



# Testbench

```
module testbench;

    reg clk;
    reg rst;
    reg dataready;
    reg [7:0] Data_in;
    reg receiveData;

    wire [7:0] Data_out;
    wire OutBuffFull;
    wire error;
    wire readyToAccept;

    System uut (
        .clk(clk),
        .rst(rst),
        .dataready(dataready),
        .Data_in(Data_in),
        .receiveData(receiveData),
        .Data_out(Data_out),
        .OutBuffFull(OutBuffFull),
        .error(error),
        .readyToAccept(readyToAccept)
    );

    always #5 clk = ~clk;

    initial begin
        clk = 0;
        rst = 0;
        dataready = 0;
        receiveData = 0;

        #6; rst = 1; #6; rst = 0;
```

```
        #20;
        dataready = 1;
        Data_in = 8'b00101101;
        #20;
        if (readyToAccept)
            dataready = 0;
        #20;
        dataready = 1;
        Data_in = 8'b00000000;
        #10;
        if (readyToAccept)
            dataready = 0;
        #20;
        dataready = 1;
        Data_in = 8'b00000111;
        #10;
        if (readyToAccept)
            dataready = 0;
        #20;
        dataready = 1;
        Data_in = 8'b00000000;
        #10;
        if (readyToAccept)
            dataready = 0;
```

```
        #200;

        if (OutBuffFull)
            receiveData = 1;
        #10;
        receiveData = 0;
        #10;
        if (OutBuffFull)
            receiveData = 1;
        #10;
        receiveData = 0;
        #10;
        if (OutBuffFull)
            receiveData = 1;
        #10;
        receiveData = 0;
        #10;
        if (OutBuffFull)
            receiveData = 1;
        #10;
        receiveData = 0;
```

```
        #100; #6; rst = 1; #6; rst = 0;

        #20;
        dataready = 1;
        Data_in = 8'b00000011;
        #20;
        if (readyToAccept)
            dataready = 0;
        #20;
        dataready = 1;
        Data_in = 8'b00000001;
        #10;
        if (readyToAccept)
            dataready = 0;
        #20;
        dataready = 1;
        Data_in = 8'b00000010;
        #10;
        if (readyToAccept)
            dataready = 0;
        #20;
        dataready = 1;
        Data_in = 8'b00000001;
        #10;
        if (readyToAccept)
            dataready = 0;
```

```
        #200;





        if (OutBuffFull)
            receiveData = 1;
        #10;
        receiveData = 0;
        #10;
        if (OutBuffFull)
            receiveData = 1;
        #10;
        receiveData = 0;
        #10;
        if (OutBuffFull)
            receiveData = 1;
        #10;
        receiveData = 0;
        #10;
        if (OutBuffFull)
            receiveData = 1;
        #10;
        receiveData = 0;

        #100;
        $stop;

    end

endmodule
```

# Wave Forms

    



# Post Simulation

